


Module 2 Assignment

7nm FinFET Device and Inverter Characteristics

-> For my username (rlvsk) the ASCII sum in V is 0.562.


-> So I have taken the voltage of V2 as 0.562 V.

1. VTC Curve

 


- This curve shows the relation between the input and output voltage of the inverter.
- V_{th} – is the point where both the curves intersect.
- $V_{th} = 0.273$ V


2. Drain Current (I_d) = 123.083uA

 

3. Transconductance (g_m)

 

4. Output Resistance (r_{out})

 

5. Max Gain, Noise Margin & Transconductance

```
No. of Data Rows : 701
v_th          = 2.735608e-01
max_gain      = 7.542514e+00 at= 2.760000e-01
vil           = 2.755041e-01
voh           = 2.589595e-01
vih           = 2.774596e-01
vol           = 2.442102e-01
v_th = 2.735608e-01
max_gain = 7.542514e+00
vil = 2.755041e-01
voh = 2.589595e-01
vih = 2.774596e-01
vol = 2.442102e-01
nmh = -1.85001e-02
nml = 3.129390e-02
gm_max        = 9.319728e-04 at= 3.270000e-01
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
```

6. Power Consumption and Propagation Delay

```
Initial Transient Solution
-----

Node                                Voltage
----                                -
nfet_out                            0.561735
nfet_in                             0
vdd                                  0.562
v2#branch                           -5.37516e-07
v1#branch                           7.70734e-12

Reference value : 0.00000e+00
No. of Data Rows : 120
tpr = 2.500000e-11
tpf = 2.443827e-11
id_pwr = -6.96304e-16 from= 2.00000e-11 to= 6.00000e-11
tpr = 2.500000e-11
tpf = 2.443827e-11
tp = 2.471913e-11
id_pwr = -6.96304e-16
pwr = -3.91323e-16
power = 9.783070e-06
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Using SPARSE 1.3 as Direct Linear Solver
```

7. Frequency

```
Initial Transient Solution
-----

Node                                Voltage
----                                -
nfet_out                            0.561735
nfet_in                             0
vdd                                  0.562
v2#branch                           -5.37516e-07
v1#branch                           7.70734e-12

No. of Data Rows : 71
tr = 2.080000e-11
tf = 2.318204e-11
t_delay = 4.398204e-11
f = 2.273655e+10
```

Characteristic Table:

S.No	W/L (PMOS)	W/L (NMOS)	V _{th} (V)	I _d (uA)	P (W)	t _{pd} (ps)	A _v	f (Hz)
1	2.00	2.00	0.2735608	123.083	9.78307E-06	2.47191E-11	7.572514	22736550000
2	1.00	1.85	0.2454671	82.35	6.70E-06	2.45E-11	7.730707	2.28E+10
3	1.85	1	0.3020096	80	6.71E-06	2.50E-11	7.494735	2.26E+10

Observations:

Effect of Increasing NMOS width

- Strengthens the channel conduction, leading to larger discharge current.
- Output node pulls down quicker, resulting in shorter falling delay.
- Switching occurs sooner as the effective threshold voltage moves slightly lower.

Effect of Increasing PMOS width

- Improves the ability to charge the output node, causing higher charging current.
- Output rises faster, giving smaller rising delay.
- Devices switches later as the threshold point shifts upwards.
- Overall power usage becomes greater due to increases current flow.

Balances PMOS and NMOS Sizing

- Pull-up and pull-down paths show similar driving capability.
- The inverter toggles close to half of the supply voltage ($V_{DD}/2$).
- Rise and fall delays become almost equal.
- Provides a good compromise between performance and power efficiency.